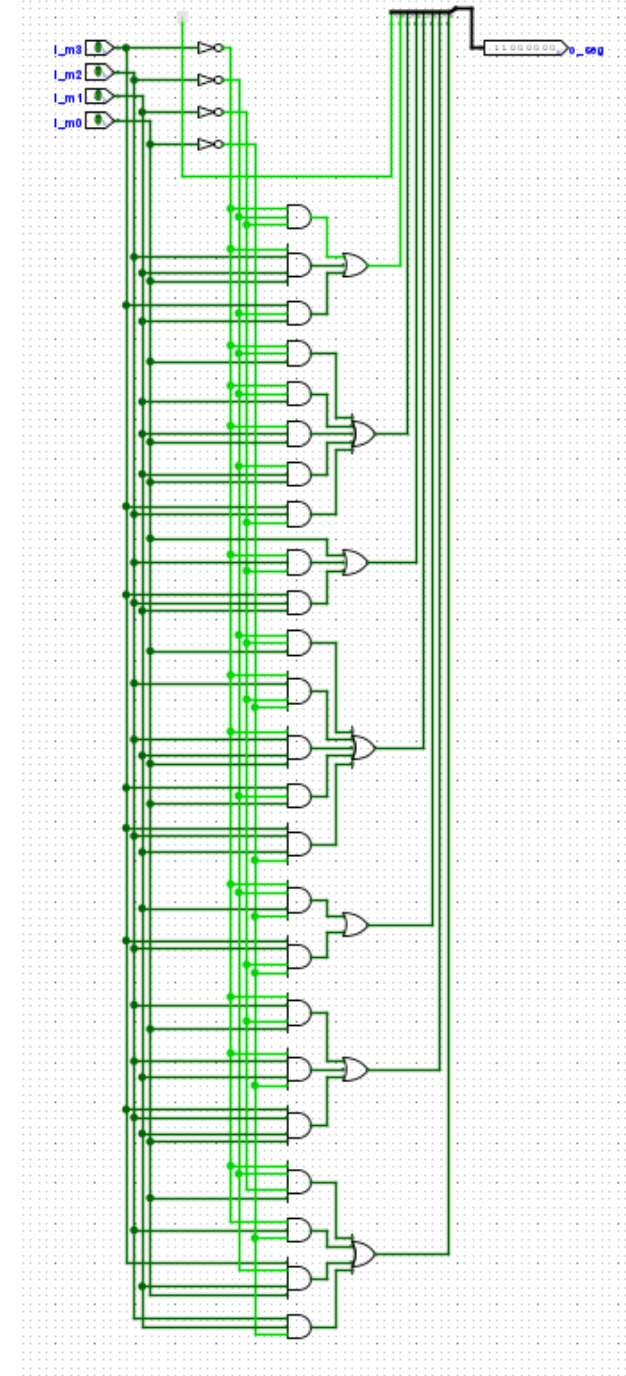



7 Segment Decoder

- When overflows from 9 to 10 we return to 0

0	$\Pi(0, 1, 2, 3, 4, 5)$
1	$\Pi(1, 2)$
2	$\Pi(0, 1, 3, 4, 6)$
3	$\Pi(0, 1, 2, 3, 6)$
4	$\Pi(1, 2, 5, 6)$
5	$\Pi(0, 2, 3, 5, 6)$
6	$\Pi(2, 3, 4, 5, 6)$
7	$\Pi(0, 1, 2)$
8	$\Pi(0, 1, 2, 3, 4, 5, 6)$
9	$\Pi(0, 1, 2, 5, 6)$




Circuit B

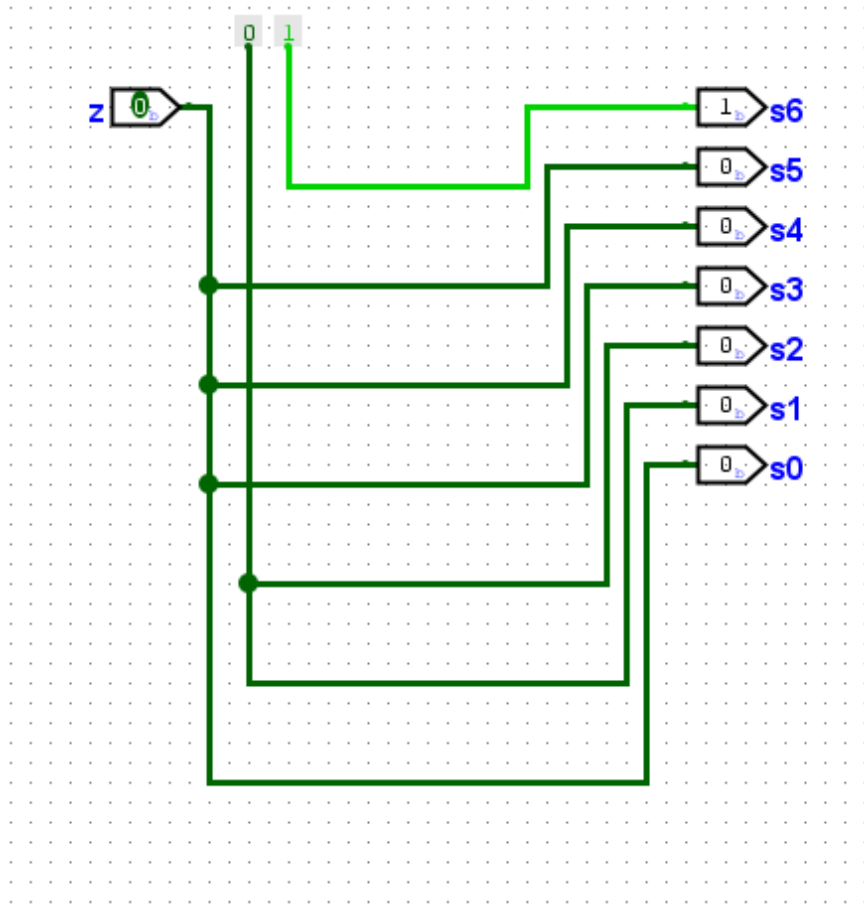

When Z is 0 the output produces a 0 on the 7 segment
When Z is 1 the output produces a 1 on the 7 segment

Comparator

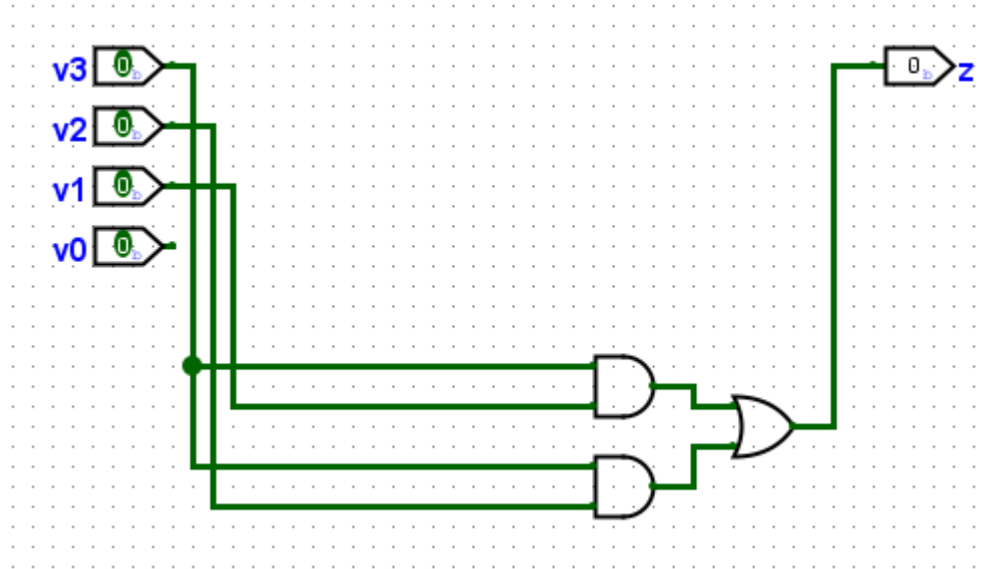

When the value is 9 or less Z is 0

When the value is 10 or greater Z is 1