



Down Counter From 3 to 0

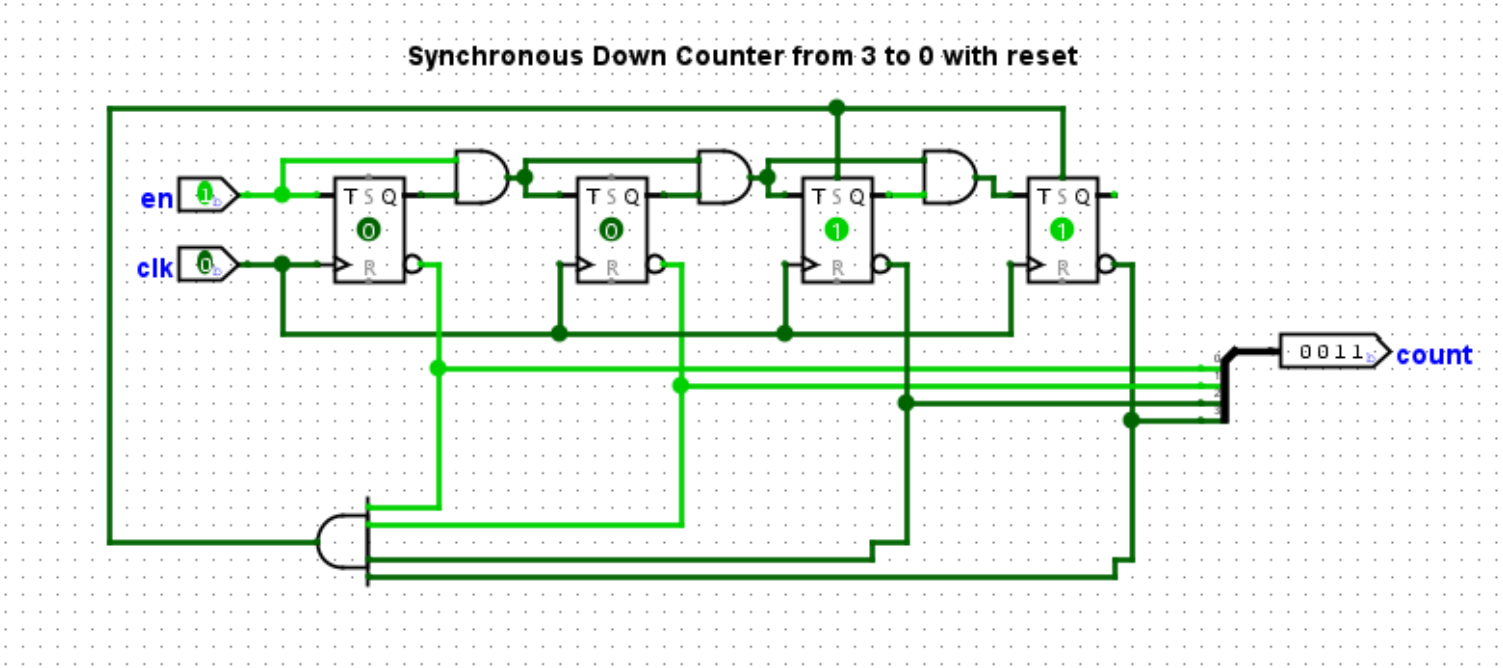

State Machine

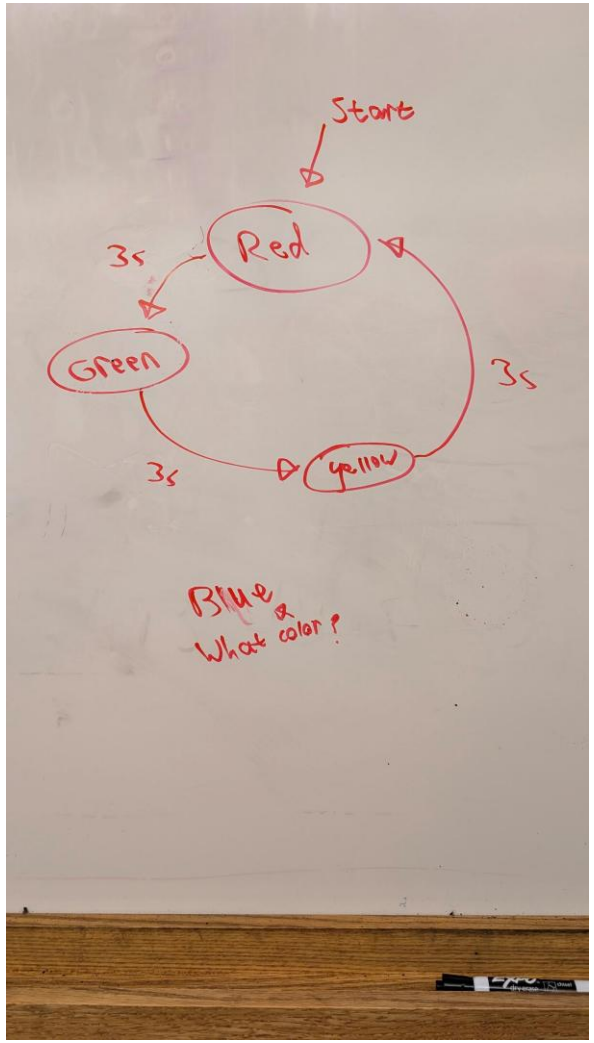


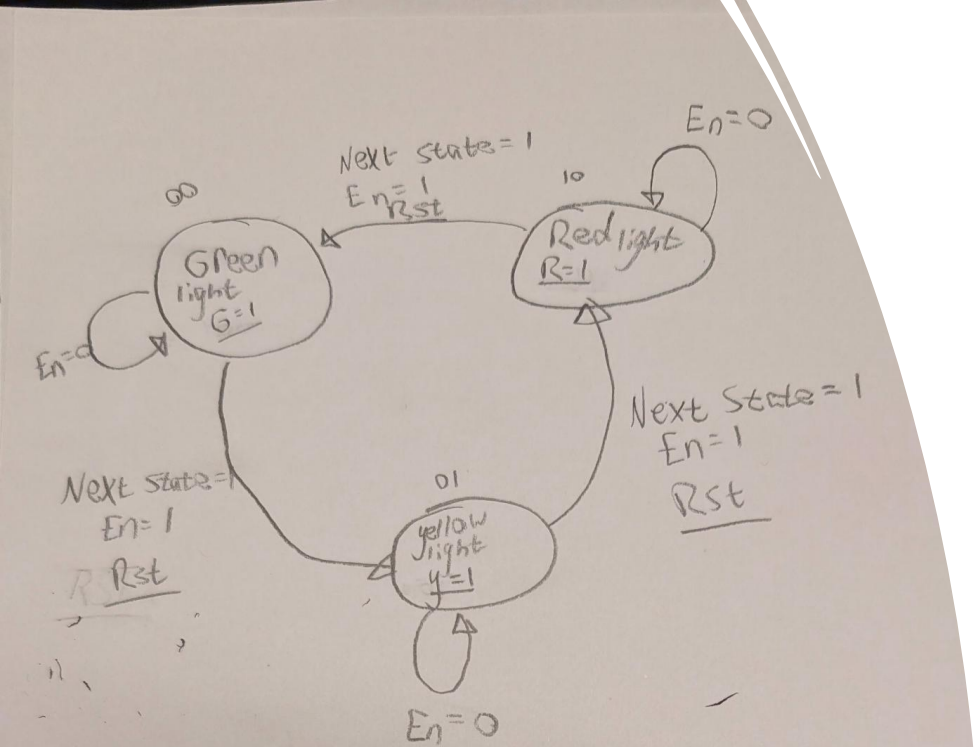

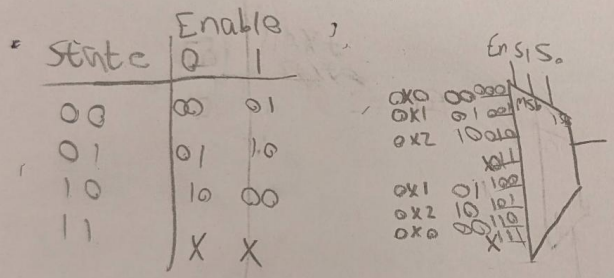

Modified State Diagram and Truth Table

FSM Initial Design

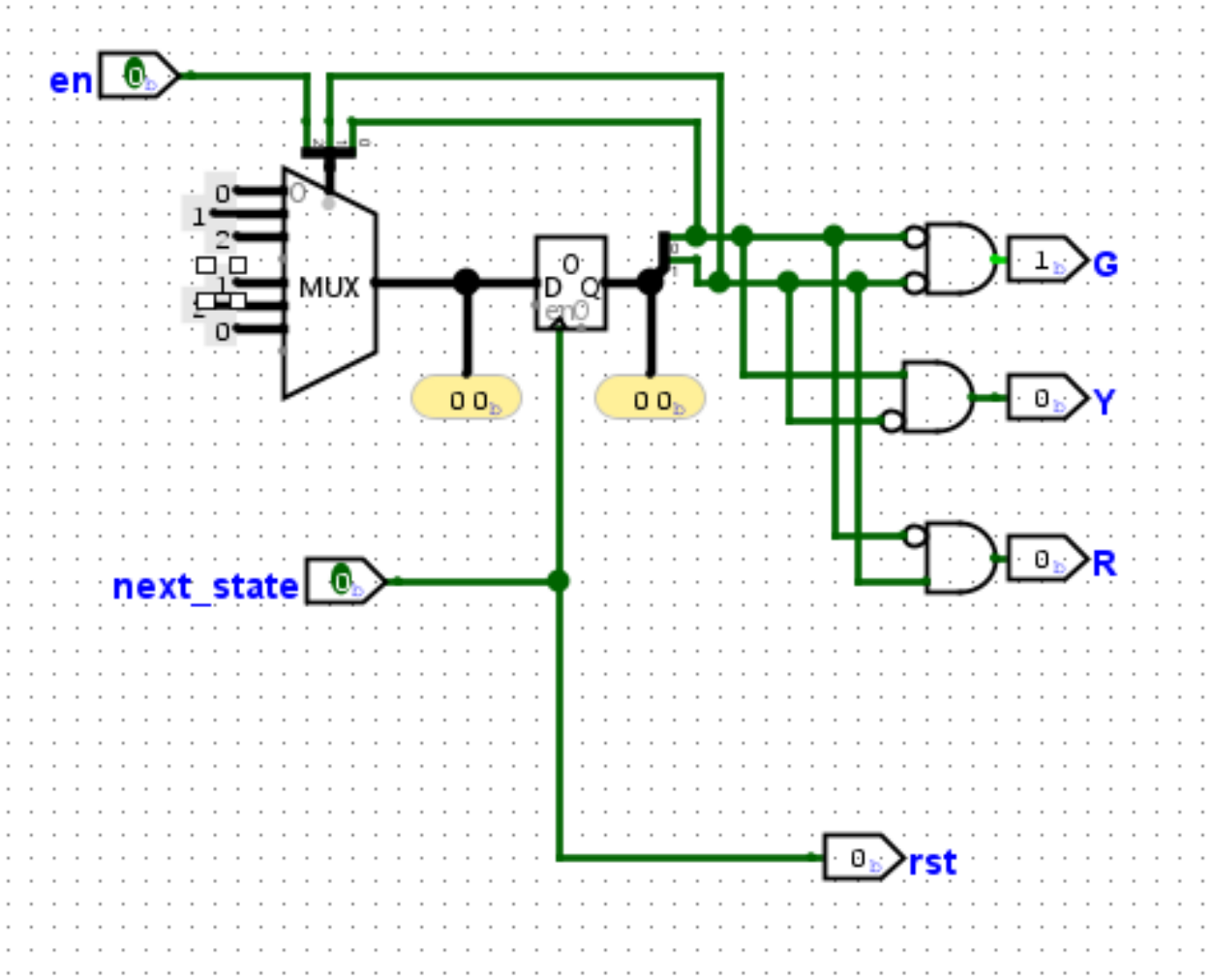

Functioning Traffic Light

