
Final Project


Pedestrian Walk Request Circuit

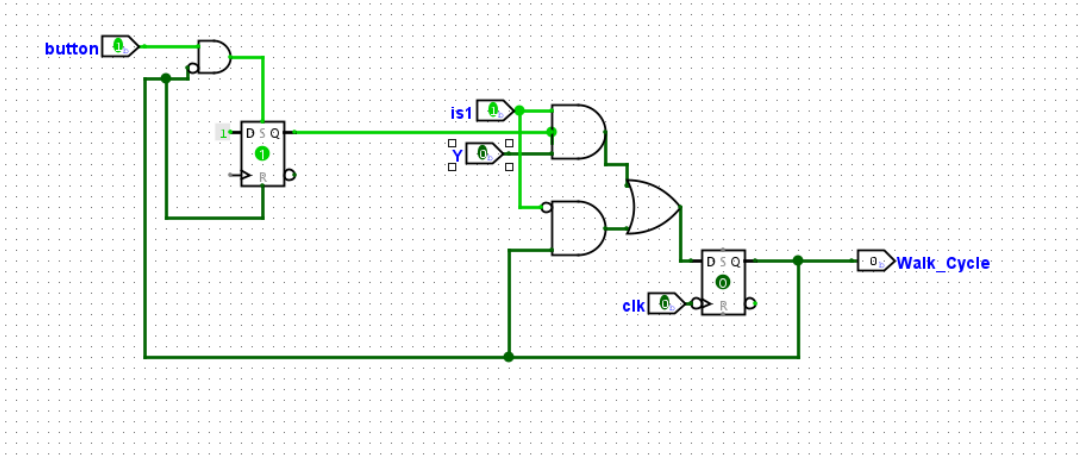- The button input combined with not walk means that it does not take request while walk is active
- Is1 makes sure that it goes live before the color switches at zero
- Y checks if the light color is yellow to ensure the walk cycle lands on red
- The NOT is1 AND walk_cycle is to ensure that walk_cycle stays live when the counter goes to 0




ls1 Circuit

- This is just checking count = 1

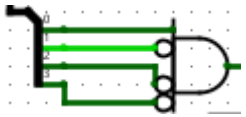

Main Circuit With Request Integrated

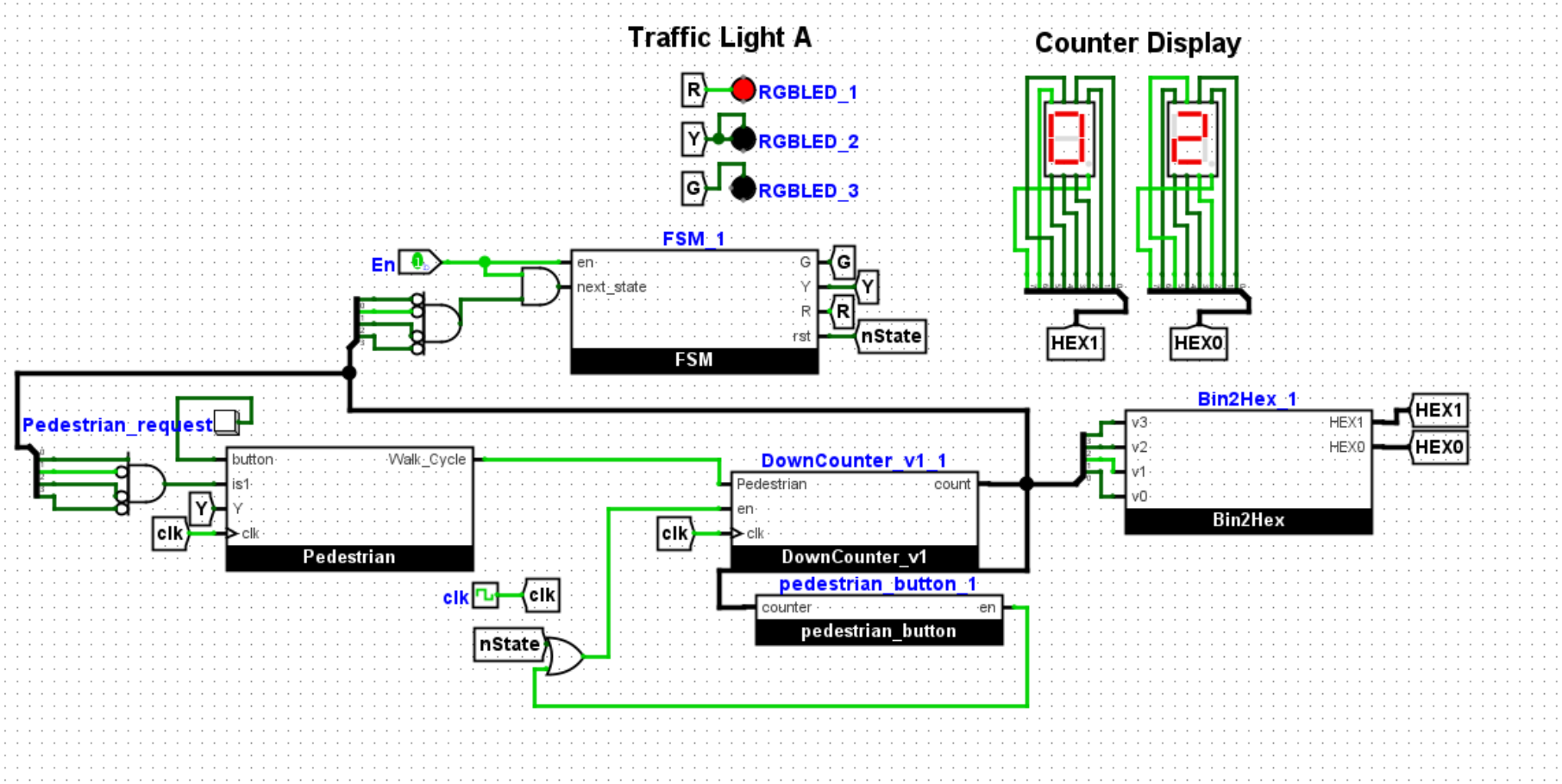

Adjusted Down Counter

- The counter has been adjusted to take an extra input so it can switch the set point to 10 (1010) instead of 3 (0011) whenever the walk signal is on

